1 Exercise 2

Having the function in maxterms

$$f_1(A, B, C, D) = \prod (M_0, M_1, M_5, M_7, M_8, M_{10}, M_{14}, M_{15})$$

equivalent to

$$f_2(A, B, C, D) = \sum (m_2, m_3, m_4, m_6, m_9, m_{11}, m_{12}, m_{13})$$

using minterms, can be simplify by different ways and represented using logic gates.

1.1 Boolean Algebra

Using the Boolean algebra propertie

$$(A+B).(A+\overline{B}) = A (1)$$

or

$$(AB) + (A\overline{B}) = A (2)$$

the function could be simplify using (1):

$$f_1(A, B, C, D) = (A + B + C + D).(A + B + C + \overline{D}).(A + \overline{B} + C + \overline{D}).(A + \overline{B} + \overline{C} + \overline{D}).$$

$$(\overline{A} + B + C + D).(\overline{A} + B + \overline{C} + D).(\overline{A} + \overline{B} + \overline{C} + D).(\overline{A} + \overline{B} + \overline{C} + \overline{D})$$

$$= (A + B + C).(A + \overline{B} + \overline{D}).(\overline{A} + B + D).(\overline{A} + \overline{B} + \overline{C})$$

Which in minterms would be, using (2):

$$f_{2}(A, B, C, D) = (\overline{ABCD}) + (\overline{ABC})$$

$$= (A\overline{BD}) + (\overline{ABD}) + (\overline{ABC}) + (\overline{ABC})$$

1.2 Karnaugh Map

Karnaugh map is a easier way to simplify logic experesion when the functions are too complex or too large to handle, cause Karnaugh map gives a more representative view for a faster analysis for it to simplify.

CD A	B 00	01	11	10
00	0	1	1	0
01	0	0	1	1
11	1	0	0	1
10	1	1	0	0

Now grouping the colour groups we get that the function in minterms would be:

$$f_2(A, B, C, D) = (A\overline{B}D) (Red)$$

 $+(\overline{A}B\overline{D}) (Blue)$
 $+(\overline{AB}C) (Orange)$
 $+(AB\overline{C}) (Green)$